

Project 2

In this section we are suppose to add/Subtract two binary Values.

Here's a small intro to what Binary numbers are & how to convert it to decimal & vice-versa.

Binary Numbers look like this 0101001101. This is because down to chip level, computers just understand on or off.

Convert Binary to Decimal

2^9	2^8	2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0
1	1	1	0	0	1	0	1	0	1

Step 1 for each box multiply the value with the power of 2 mentioned above

U'll get something like this

X → → → →	512	0	128	64	0	0	8	0	2	0
-----------	-----	---	-----	----	---	---	---	---	---	---

2 Step 2

just add these Values

$$512 + 128 + 64 + 8 + 2 = \cancel{714}$$

Now, let's go the other way around

Decimal to Binary

Step 1 Divide 714 by 2 $\rightarrow 2 \overline{)714} - 0$
& store the difference $2 \overline{)357} - 1$
 $2 \overline{)178} - 0$

Step 2 Arrange them from
Bottom to top $2 \overline{)89} - 1$
 $2 \overline{)44} - 0$
 $2 \overline{)22} - 0$
 $2 \overline{)11} - 1$
 $2 \overline{)5} - 1$
 $2 \overline{)2} - 0$

$$\rightarrow 101100101$$

$$\begin{array}{r} 714 \\ \hline 101100101 \end{array}$$

ADDITION

$$\begin{array}{r} 0111101 \\ + 0011010 \\ \hline 1010111 \end{array}$$

1+1 = $\boxed{0}0$ \hookrightarrow 1 Carry Over

$1+1+1 = \boxed{1}1$ \hookrightarrow 1 Carry Over



There are three chips to add Binary
Numbers
 \rightarrow Half Adder

- '0'
- Full Adder
- Adder

Let's Start with Half Adder

Half Adder has 2 inputs $\rightarrow a, b$
 $\& 2$ outputs \rightarrow Carry, Sum

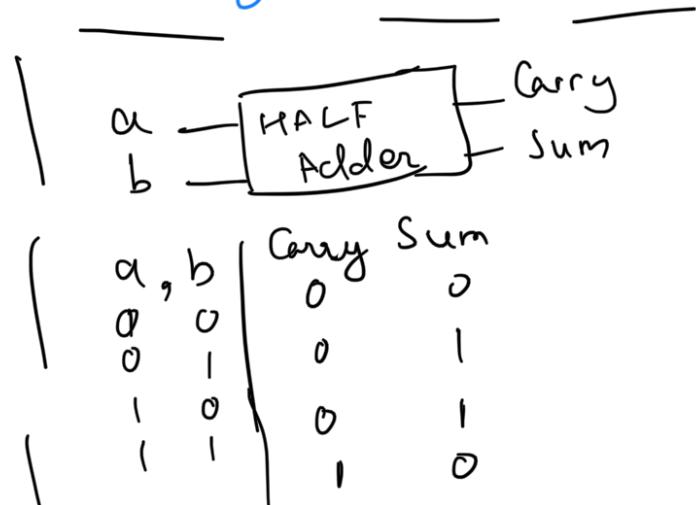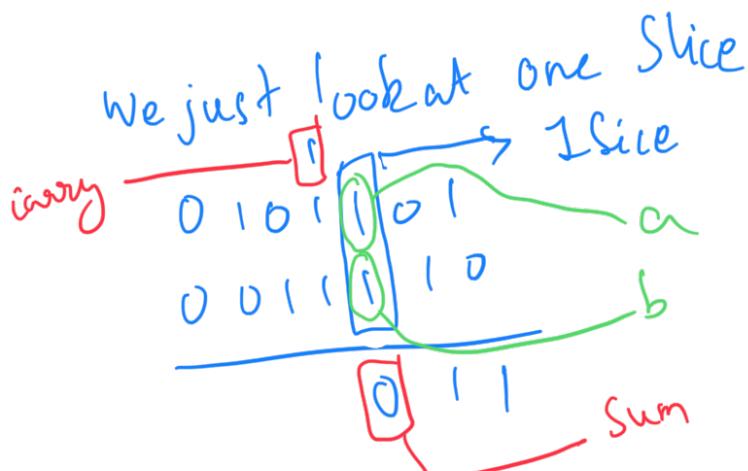
notice that we don't care about the carry from previous slice



Try this one, it's pretty simple


Carry is just Add ($a=a, b=b, \text{out}=\text{carry}$)
 $\&$ Sum is just xor ($a=a, b=b, \text{out}=\text{sum}$)

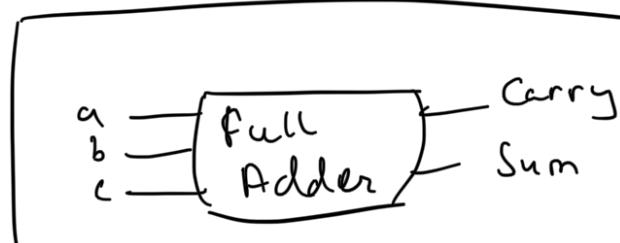Full Adder
 \rightarrow 3 inputs a, b, c
 \rightarrow 2 out Carry Sum



In full adder we can add 3 bits, but we are still dealing with One Slice

- 1 bin | $a \ b \ c$ | Sum Carry

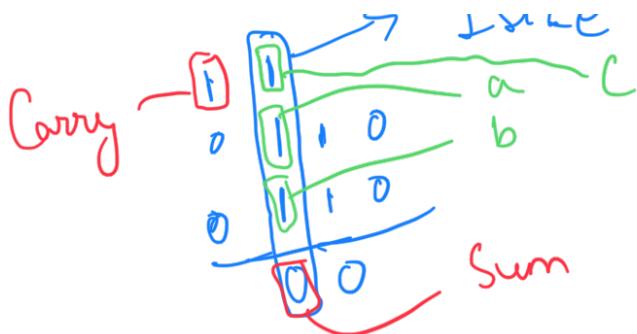

a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

temp Sum, temp Carry

0	0
1	0
1	1
0	1

Sum, Carry

1	0
0	1
0	1
1	1

Sum or temp Carry

0	0
1	0
0	0

→
0
1
;

There may exist
a better way of
doing this, below
is the method I came
up with.

<first use HalfAdder($a=b$, $b=c$, $sum=tempSum$, $carry=tempCarry$);

temp blog we are not sure yet

then we use

$\text{Not}(\text{in}=tempSum, \text{out}=tempSum2);$

bcoz this is the other half of sum & we
are not sure which one is correct.

We finally use $Mux(a=tempSum, b=tempSum2, sel=a, out=Sum);$


we finally get the desired
sum result

then we do the $Or(a=tempSum, b=tempCarry, out=tempCarry2);$

this is to get the desired carry2
-


then we finally choose one of two "Carry"

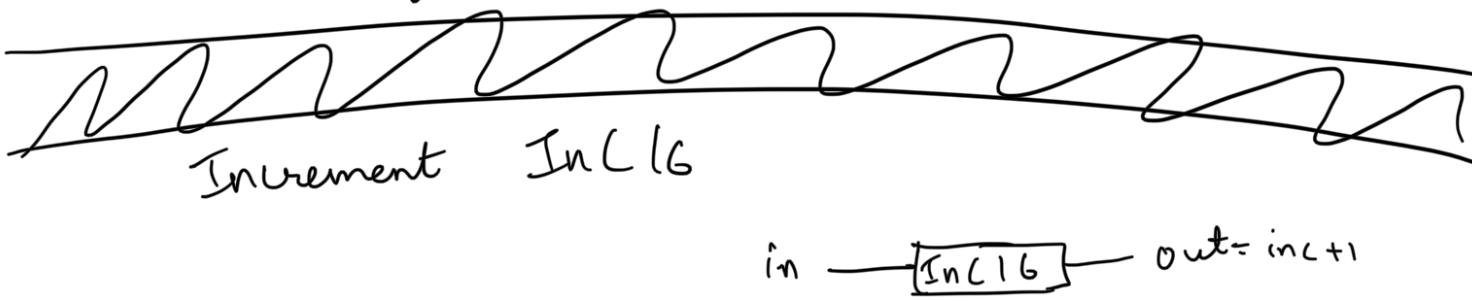Mux C a=templay, b= temp carry 2, sel=a, out=carry);



Add16[a=in, b[0]=true, out=out];

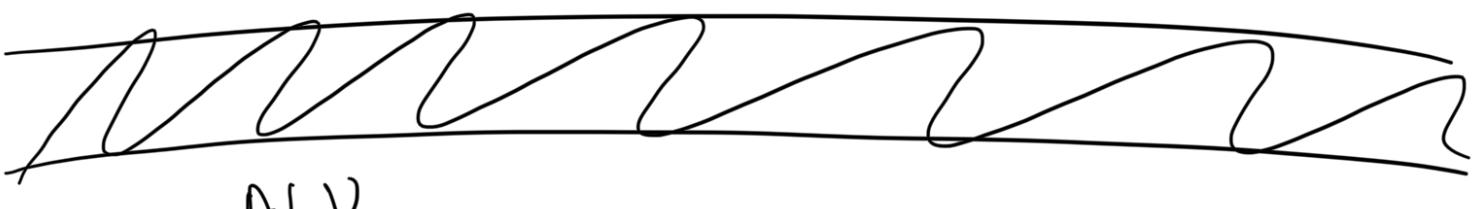$[0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 1]$
adds this to in



IN- $x[16], y[16]$


Out = Out[16]

Zr

ng

Zx
Nx
Zy
Ny
f
no

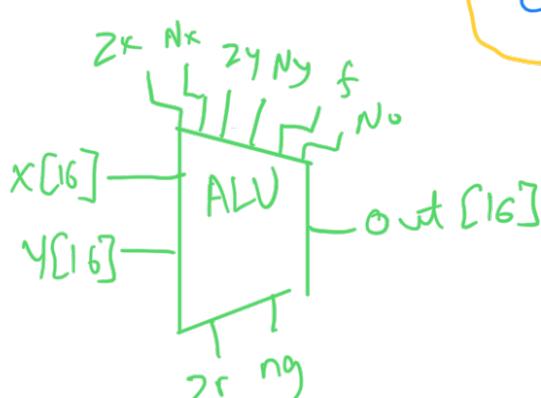ALU is the Biggest Chip yet
but it is simpler than it looks
just follow the below rules & you
can easily make it



The Hack ALU operation

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

- ↑ Do the tasks in the given order, don't worry much about the truth table
- ↑ Change the X values to 0 if $Z \times 1$ - Use this new X moving forward
if $N \times 1$ change the new X to $\neg X \rightarrow$ Use this as new X

Do same with Y.

→ Calculate both $X+Y$ & $X \& Y$ now use MUX to decide which one we need. Store this out in a temp variable

→ Calculate Not of temp output & use MUX to decide if we should put final output as Notout or out.

 Create two outputs so that we can use one to out pin & use other to calculate Z_r & N_g

Z_r is 1 if $out == 0$ else 0

N_g is 1 if $out < 0$ or 0

for N_g → Output is 1 when output[15] is 1. So we will use output[15] as Sel for MUX and use a & b as true or false

for Z_r → Output is 0 when none of its 16 bits contain 1. Some need to use Or to check that. If the output of Or is 1, number is not 0 else it is 0

 for Z_r I tried using 2 Or 8Way & 1 Or to get the final Or output. But that may be complicated b'z you will create a lot of variables. So I created a Or 16Way chip to minimize the process. Do the same]

Below is the code if you couldn't understand.

```
CHIP ALU {
    IN
        x[16], y[16], // 16-bit inputs
        zx, // zero the x input?
        nx, // negate the x input?
        zy, // zero the y input?
        ny, // negate the y input?
        f, // compute out = x + y (if 1) or x & y (if 0)
        no; // negate the out output?

    OUT
        out[16], // 16-bit output
        zr, // 1 if (out == 0), 0 otherwise
        ng; // 1 if (out < 0), 0 otherwise

    PARTS:
        Mux16(a=x,b=false,sel=zx,out=X);
        Not16(in=X,out=NotX);
        Mux16(a=X,b=NotX,sel=nx,out=zX);

        Mux16(a=y,b=false,sel=zy,out=Y);
        Not16(in=Y,out=NotY);
        Mux16(a=Y,b=NotY,sel=ny,out=zY);

        Add16(a=zX,b=zY,out=XplusY);
        And16(a=zX,b=zY,out=XAndY);
        Mux16(a=XAndY,b=XplusY,sel=f,out=F);

        Not16(in=F,out=NotF);
        Mux16(a=F,b=NotF,sel=no,out=out,out=outcopy,out[15]=outcopy2);

        Or16Way(in=outcopy,out=notzr);
        Not(in=notzr,out=zr);

        Mux(a=false,b=true,sel=outcopy2,out=ng);
```