

Project 1

NAND

| x | y | f |
|-----|-----|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

→ $\text{Not}(x) \& \text{Not}(y)$
 → $\text{Not}(x) \& y$
 → $x \& \text{Not}(y)$

$(\text{Not}(x) \& \text{Not}(y))$ $(\text{Not}(x) \& y)$ or $(x \& \text{Not}(y))$


$\text{Not}(x \& y)$



XOR

| x | y | f |
|-----|-----|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

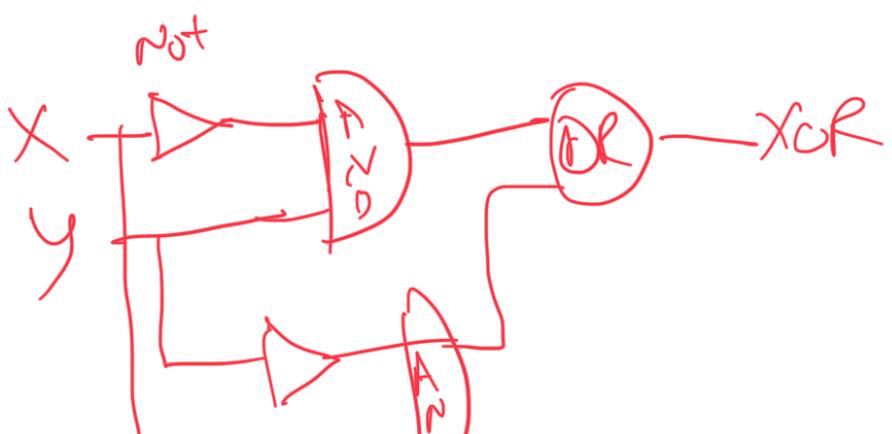- $\text{Not}(x) \& y$
 - $\text{Not}(y) \& x$



19

AND

| x | y | And |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

NAND

| x | y | NAND(x,y) |
|---|---|-----------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

NAND(NAND(x,y), x)

| y | x | NAND(x,y) | f | f(Nand(x,y), y) |
|---|---|-----------|---|-----------------|
| 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |

Not Gate

| x | Not(y) |
|---|--------|
| 0 | 1 |

NAND

| x | y | Nand(x,x) |
|---|---|-----------|
| 0 | 0 | 1 |

| | | |
|---|---|---|
| 1 | 1 | 0 |
|---|---|---|

| | | | |
|---|---|---|---|
| 1 | 1 | 1 | 0 |
|---|---|---|---|

XOR GATE

| X | Y | f |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

$\text{And}(\text{Not}(x), y) \text{ OR } \text{Not}(y) \text{ AND }$

OR

| X | Y | OR |
|---|---|----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

$\text{And}(\text{Not}(x), y)$

OR

$\text{And}(\text{Not}(y), x)$

OR

$(\bar{x}) \cdot (\bar{y})$

NAND

| X | Y | NAND |
|---|---|------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

$\text{And} = \text{Nand}(\text{Nand}(x, y), \text{Nand}(x, y))$

| X, Y, !X, !Y | Nand |
|--------------|------|
| 0, 0, 1, 1 | 0 |
| 0, 1, 1, 0 | 1 |
| 1, 0, 0, 1 | 1 |
| 1, 1, 0, 0 | 1 |

MUX (Multiplexor)

3 Inputs \rightarrow a, b, Sel

| Sel | out |
|-----|-----|
| 0 | a |
| 1 | b |

$a \& \text{Not}(b)$

$a \& \bar{b}$

$\text{Not}(a) \& b$

$a \& b$

| a | b | Sel | Mux |
|---|---|-----|-----|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 |

$a \& \text{Not}(b) \& \text{Not}(c)$

$a \& b \& \text{Not } c$

$\text{Not } a \& b \& c$

$a \& b \& c$

| a | Sel | Not Sel |
|---|-----|---------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |


And (a, Not Sel)

- 0 ✓
- 0 ✓
- 1 ✓
- 0 ✓

we want
0 1 0 0
0 0 1 0
1 0 0 0
0 1 0 1



& Find out
(b, Not Sel),

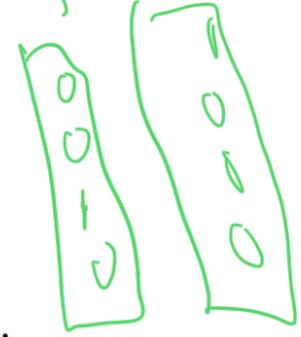

| b | Sel | Not Sel |
|---|-----|---------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| a, b, Sel | $A \wedge \text{Not Sel}$ | $B \wedge \text{Not Sel}$ | Desired |
|-------------|---------------------------|---------------------------|---------|
| 0 0 0 | 0 | 0 | 0 |
| 0 0 1 | 0 | 0 | 0 |
| 0 1 0 | 0 | 1 | 0 |
| 0 1 1 | 0 | 0 | 1 |
| 1 0 0 | 1 | 0 | 1 |
| 1 0 1 | 0 | 0 | 0 |
| 1 1 0 | 0 | 1 | 1 |
| 1 1 1 | 0 | 0 | 1 |

| X | Y | D | Arranged |
|-------|---|---|----------|
| 0 0 0 | 0 | 1 | 0 0 → 1 |
| 0 0 0 | 0 | 0 | 0 0 → 0 |
| 0 1 0 | 0 | 1 | 1 0 → 1 |
| 0 0 1 | 1 | 1 | 1 1 → 1 |
| 1 0 1 | 1 | 1 | |
| 0 0 0 | 0 | 0 | |
| 1 1 1 | 1 | 1 | |
| 0 0 1 | 0 | 1 | |

DMUX

Input - Sel, in
Output - a, b

if $sel = 0$
output = $in_0, 0$
else
 $out = 0, in$

| In | Sel | Out |
|----|-----|-----|
| 0 | 0 | 00 |
| 0 | 1 | 00 |
| 1 | 0 | 10 |
| 1 | 1 | 01 |

In Mux

```

if sel = 0
    out = a
else
    out = b
  
```

XGATE

D Mux($a = \text{in}$, $b = 0$, Sel, out=a)

| MUX | | | | | Desired | |
|-----|-----|---|---|----|---------|---|
| in | Sel | a | b | MO | a | b |
| 0 | 0 | 0 | 1 | 6 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |


Or 16, And 16, Mux 16 are easy
Same thing again again

MUX 4 WAY 16

1. Implement Mux 4 Way with just 1 bit



lets first 'i')

in = a, b, c, d, Sel, Sel2

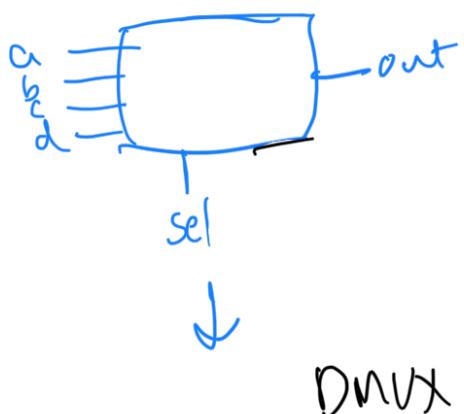

| Sel | x | y |
|-----|---|---|
| 00 | 1 | 0 |
| 01 | 0 | 1 |
| 10 | 1 | 1 |
| 11 | 0 | 0 |

let a, b be x
let c, d be y

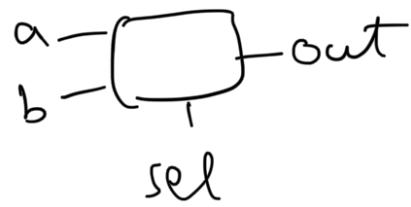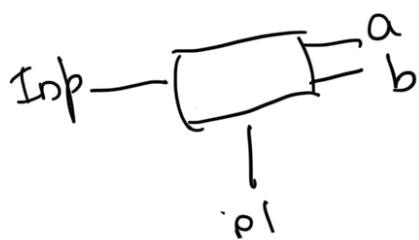

②

Now find for c, d.

This can be done by

Mux¹⁶(a=c, b=d, Sel=Sel[0])

Store it in temp 1

first complete for a, b
which be done using
Mux¹⁶(a=a, b=b, Sel=Sel[0])
store it in temp 1

bcoz
a, b are only
chosen when
Sel is [01] or [10]
So we only
care abt Sel[0]

bcoz c & d are only

called when Sel is [10] or [11]

Remember that in reality

there are just 2 bits for sel

and exists 4 possible states

| | |
|---|---|
| 0 | 0 |
| 0 | 1 |
| 1 | 0 |
| 1 | 1 |

c. I.e. same we get Sel = 10,


our temp 1 will choose [a]
 but our temp 2 should choose [c]
 On the other hand if sel = 11, temp 1 = b
 & temp 2 should be d. Did You Get it!!
 we just need to use the mux for c & d with
 sel[0]!

Now we need to choose b/w temp 1 &
 temp 2 • if you look closely temp 1 is
 always chosen when Sel = 00 or 01. Basically
 when Sel[1] = 0 temp 1 is chosen & when Sel[1] is
 1 we need temp 2!

So just use Mux 16(a=temp 1, b=temp 2, Sel=Sel[1], out_{out})

Voila!

MUX 8 Way 16!!!

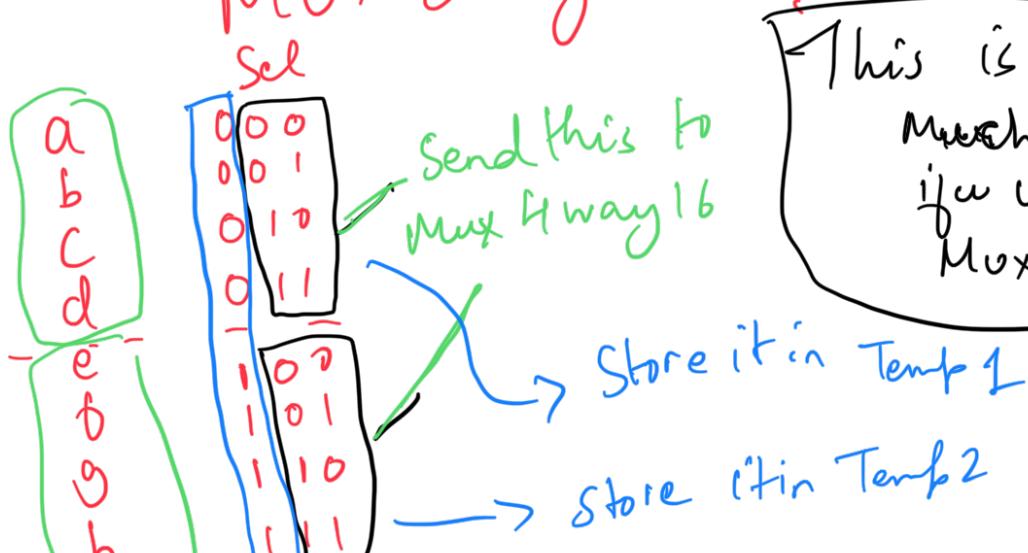

This is actually
 much easier
 if u understand
 Mux 4 Way 16

LOOK AT
 MUX4WAY16
 for better

U
W


Now to choose b/w temp 1 & temp 2

Use this

Understanding



DMux 4 Way

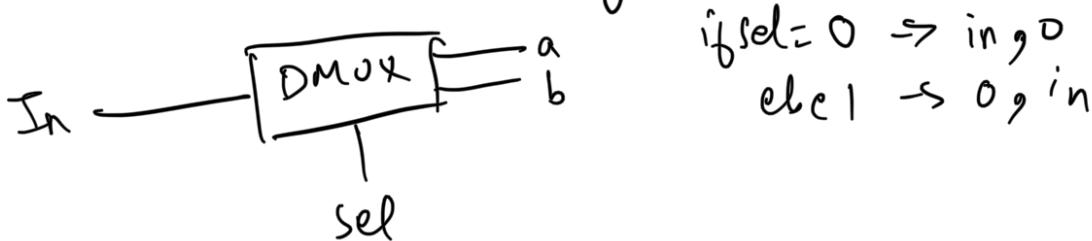

2 Inputs \rightarrow in, Sel (2)
 4 outputs $\rightarrow a, b, c, d$

| | | | | |
|----|----|----|----|----------|
| in | 0 | 0 | 0 | sel = 00 |
| 0 | in | 0 | 0 | 01 |
| 0 | 0 | in | 0 | 10 |
| 0 | 0 | 0 | in | 11 |

Similar to the way we solved Mux 4 Way^(b), Here also we will first solve for a & b

So \rightarrow DMux ($in = in$, $Sel = Sel[0]$, $a = temp_a$, $b = temp_b$)

this will give us $in, 0$
 or
 $0, in$

Now, as a & b can just be 0s

So to check that we need to look

at $Sel[1]$. We find that whenever $Sel[1]$ is 0, a & b can have "in" val. at $Sel = [0]0, [0]1$. But whenever $Sel[1]$ is 1, a & b are guaranteed to be 0. at $Sel[1]1$

\dots and $in \leq L \leq 1$

temp bcoz we are not sure with the vals yet, as they can just be 0s

So Now we need to use DMux

DMux (in=tempa, Sel=Sel[1], a=a, b=c)

this bcoz if sel[1] is 0, a will be tempa
and that would mean it will have in value
so naturally c will be 0!

Same this is true for b & d

DMux (in=tempb, Sel=Sel[1], a=b, b=d)

DMux 8 Way

| | in | 0 0 0 0 0 0 0 0 | Sel = | 0 0 0 |
|---|----|------------------|-------|-------|
| a | 0 | in 0 0 0 0 0 0 0 | | 0 0 1 |
| b | 0 | 0 in 0 0 0 0 0 0 | | 0 1 0 |
| c | 0 | 0 0 in 0 0 0 0 0 | | 0 1 1 |
| d | : | | | 1 0 0 |
| e | : | | | 1 0 1 |
| f | ; | 0 0 0 0 0 in 0 0 | | 1 1 0 |
| g | | 0 0 0 0 0 0 in 0 | | 1 1 1 |
| h | | 0 0 0 0 0 0 0 in | | |

So I tried doing the same thing as the DMux 4 Way
but that did not work, so I did this \Rightarrow

just like we divided DMux 4 Way into 2 Port A & C
here I divided it into A & E. group A i.e. a,b,c,d only
have a chance of having "in" if $sel[2]=0$. else E group i.e. e,f,g,h
will have "in"!

So -

DMux (in=in, sel=sel[2], a=tempa, b=tempe)

if let say tempa is "in" that means $s[2]=0$ & one out of a,b,c,d has e. We don't know which one.

Bcoz we are not sure if exactly "a" or "e" are 1 or their group members

So for that -

DMux 4 Way (in=tempa, sel=sel[0..1], a=a, b=b, c=c, d=d);

if tempa is 0, which means tempe is 1, then all of abcd will be 0, which is what we want

Similarly -

DMux 4 Way (in=tempe, sel=sel[0..1], a=e, b=f, c=g, d=h)

Voila!

